

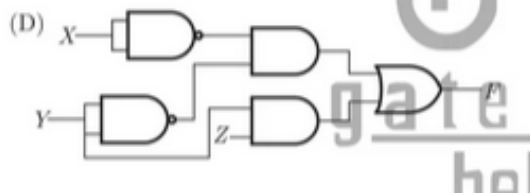
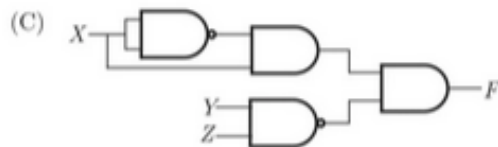


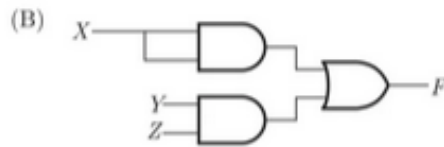Q 53). Which of the following circuits is a realization of $X'Y' + YZ$



sol: Hence, (D) is the correct option since $F = X'Y' + YZ$

In option D,

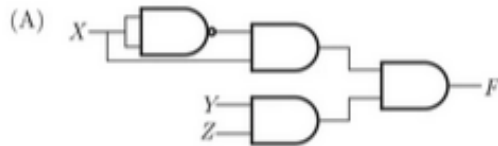