# IMPLEMENTATION OF BOOLEAN LOGIC USING ARDUINO

#### N. VARALAKSHMI


varalakshminissankara40gmail.com

#### COMET.FWC021

## Future Wireless Communication (FWC) ASSIGNMENT

July 07, 2025

#### **Abstract**

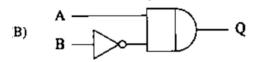

(GATE 2010 PH, Question No.41 – Implementing The above boolean function using arduino)

## 1. Components

Component	Qty
Arduino UNO Board	1
USB Cable (Type B)	1
Push Buttons	2
LEDs	1
$220\Omega$ Resistors	2
Jumper Wires (M-M)	10
Breadboard	1
Android Mobile with Ar-	1
duinodroid App	

Table 1: List of components used

## 2. Setup and Connections

1. Connect push buttons to D2, D3, for A, B.

## 5.Implementation

$$Q = \text{Minterm for } A = 1, B = 0$$
  
=  $A \cdot \overline{B}$   
=  $Q = A \cdot \overline{B}$ 

- 2. Add pull-down resistors to each input.
- 3. Connect an LED to pin D13 via a  $220\Omega$  resistor.
- 4. Common ground for buttons and LED.
- 5. Power Arduino via USB and Arduinodroid app.

## 3. Steps for Implementation

- 1. Complete the circuit connections.
- 2. Connect Arduino to mobile via USB.
- 3. Open Arduinodroid, select board and port.
- 4. Open, save, compile and upload code.

#### 4. Truth Table

A	B	F
0	0	0
0	1	0
1	0	1
1	1	0

## 6. Input and Output Pins

- A (Input) D2
- **B** (Input) D3
- **Q (Output LED)** D13

## 7. Arduino Code Link

https://github.com/varalakshmi298/ide/gate/gate\_q4.ino

